

## FINAL EXAM #2

EE347 F96

Print Your Name: \_\_\_\_\_

I observed the honor code that holds me responsible for my own work and responsible for my own actions with regard to this test.

Signature: \_\_\_\_\_

Part 1 (50 Points)	
Part 2 (25 Points)	
Part 3 (25 Points)	
Total (100 Points)	

1. Consider the following PSPICE circuit file.

\* EE 347 Final


Vin 2 0

Vdd 1 0 5.0

RL 1 3 20K

M3 3 2 0 0 NMOD1

Q1 2 2 3 CA3086

 

.MODEL NMOD1 NMOS (L=3U W=6U KP=69U GAMMA=0.37

+LAMBDA=0.06 RD=1 RS=1 VTO=1.0 TOX=0.04U

+CBD=2F CBS=2F CJ=200U CGBO=200P CGSO=40P CGDO=40P)

.MODEL PMOD1 PMOS (L=3U W=6U KP=34.5U GAMMA=0.37

+LAMBDA=0.06 RD=1 RS=1 VTO=-1.0 TOX=0.04U

+CBD=2F CBS=2F CJ=200U CGBO=200P CGSO=40P CGDO=40P)

.MODEL CA3086 NPN (BF=100 CJE=0.6p CJC=0.58p CJS=2.8p

+VJE=0.7)

.DC Vin 0.0 5.0 0.01


.OP

PROBE

.END

A) Sketch the circuit diagram corresponding to it.

 B) Build the circuit and measure the voltage transfer characteristic [VTC]. Please sketch the VTC on the axes provided below and ask your instructor to verify your measurement.



C) What is the value of  $V_M$ ?

## FINAL EXAM #6

EE347 F96

Print Your Name: \_\_\_\_\_


I observed the honor code that holds me responsible for my own work and responsible for my own actions with regard to this test.

Signature: \_\_\_\_\_

Part 1 (50 Points)	
Part 2 (25 Points)	
Part 3 (25 Points)	
Total (100 Points)	

 1. Consider the following PSPICE circuit file.

```
* EE 347 Final
Vin 3 0
Vdd 1 0 5.0
R1 3 4 10K
M2 2 3 1 1 PMOD1
Q1 2 4.0 CA3086
```



```
.MODEL NMOD1 NMOS (L=3U W=6U KP=69U GAMMA=0.37
+LAMBDA=0.06 RD=1 RS=1 VTO=1.0 TOX=0.04U
+CBD=2F CBS=2F CJ=200U CGBO=200P CGSO=40P CGDO=40P)
```


```
.MODEL PMOD1 PMOS (L=3U W=6U KP=34.5U GAMMA=0.37
+LAMBDA=0.06 RD=1 RS=1 VTO=-1.0 TOX=0.04U
+CBD=2F CBS=2F CJ=200U CGBO=200P CGSO=40P CGDO=40P)
```

```
.MODEL CA3086 NPN (BF=100 CJE=0.6p CJC=0.58p CJS=2.8p
+VJE=0.7)
```

```
.DC Vin 0.0 5.0 0.01
.OP
```

```
.PROBE
.END
```

 - A) Sketch the circuit diagram corresponding to it.
- B) Build the circuit and measure the voltage transfer characteristic [VTC]. Please sketch the VTC on the axes provided below and ask your instructor to verify your measurement.




- C) What is the value of  $V_M$ ?

2. In the laboratory experiments this quarter, you have had the opportunity to build and test several different types of digital logic gates from several logic families. Consider the following logic families: CMOS, TTL, and ECL. For each, describe at least one advantage, one disadvantage, and a typical application you might choose to use it in rather than selecting a design based on the other logic families.

CMOS	ADV.	VERY LOW POWER SMALL DEVICES = HIGH DENSITY RAIL-TO-RAIL LOGIC SWING
	DIS-AD	GENERALLY SLOWER SUSCEPTIBLE TO STATIC CHARGE COMPLEX PROCESS TECHNOLOGY COMPARED TO NMOS
	APPL	HIGH DENSITY MEANS IT'S SUITABLE FOR CPUs, MEMORY, DSP, VLSI LOW POWER IS GOOD FOR PORTABLE DEVICES
TTL		
	ADV.	WIDESPREAD, INEXPENSIVE, ROBUST, USUALLY FAST ENOUGH POWER CONSUMPTION NOT VERY FREQUENCY DEPENDENT
	DIS-AD	LOW DENSITY, DRAWS MORE POWER THAN CMOS AT LOW f CAUSES NOISE ON POWER LINES, LOW <sup>LOW</sup> NOISE MARGIN BEWARE IF $V_{CC} > 5V$
	APPLICATIONS	EVERYTHING THAT IS ROBUST AND PLUGGED INTO THE WALL. DECREASING IN POPULARITY. I/O DRIVERS, EMBEDDED SYSTEMS
ECL		
	ADV	FAST!!
	DIS-AD	SMALL LOGIC SWING. SUSCEPTIBLE TO NOISE CONSUMES LOTS OF POWER! LOW DENSITY
	APPL	WHERE SPEED IS CRUCIAL - FAST CPUs
		INTERFACING TRICKY WITH OTHER LOGIC FAMILIES

 3. A circuit has the following input and output traces:



Please determine the following times and indicate on the graphs above.

$$\left. \begin{array}{l} t_r = \underline{3.2 \text{ ns}} \\ t_f = \underline{4.8 \text{ ns}} \\ t_{PHL} = \underline{5 \text{ ns}} \\ t_{PLH} = \underline{4 \text{ ns}} \end{array} \right\} \begin{array}{l} = 0.8 \cdot (26 \text{ ns} - 22 \text{ ns}) \\ = 0.8 (8 \text{ ns} - 2 \text{ ns}) \end{array} \quad \begin{array}{l} 1 \text{ PT} \\ PER \end{array}$$

4 PTS  
EA.

What is the frequency of  $V_{in}$ ?

$$f = \frac{1}{40 \text{ ns}} = 25 \text{ MHz}$$

5 PTS